

# Analog Circuits, Sensor Readout and Conversion

## Design of a 2-stage OPAMP

Design bias voltages, currents and W/L values of the 2-stage OPAMP depicted in Fig. 1 in order to satisfy the provided specifications.

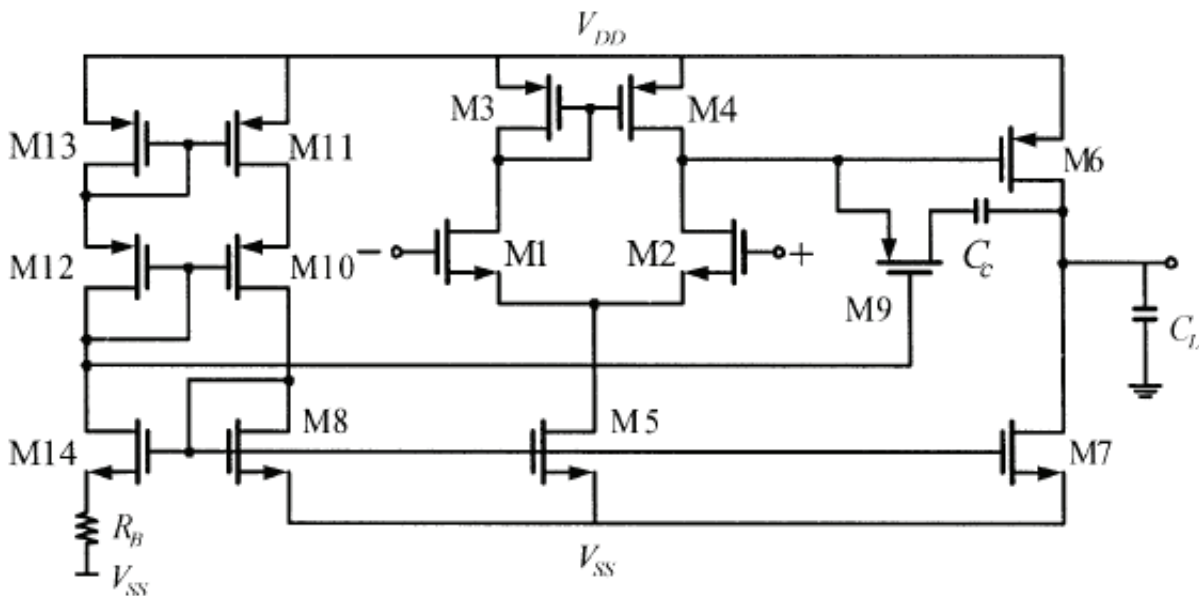


Figure 1: Op-Amp CMOS 2 stadi

- Use the following MOSFET models:

```
.model NMOD1CAP NMOS LEVEL=1
+ vto = 0.71      gamma = 0.01
+ phi = 0.6      kp= 182e-6
+ lambda = 0.01
+ tox = 9.6e-9
+ cj = 350e-6 cjsw = 120e-12
+ pb = 0.8 mj=0.33 mjsw = 0.33
+ cgso = 0.046e-9 cgdo = 0.046e-9
```

```
.model PMOD1CAP PMOS LEVEL=1
+ vto = -0.901    gamma = 0.01
+ phi = 0.6      kp= 41.5e-6
+ lambda = 0.01
+ tox = 9.6e-9
+ cj = 350e-6 cjsw = 120e-12
+ pb = 0.8 mj=0.33 mjsw = 0.33
+ cgso = 0.046e-9 cgdo = 0.046e-9
```

- **SPECS**

$V_{DD}/V_{SS}$	2.5/-2.5 V
Slew Rate	+5/-5 V/ $\mu$ s
Load Capacitor $C_L$	5pF
max Vin Common Mode	2.1V
min Vin Common Mode	-1.3V
max Vout	2.2V
min Vout	-2.2V
Gain Bandwidth	5MHz
Differential Gain	>80dB
Phase Margin	>60°

- The specification related to Noise is student-dependent. Find the value of the input-referred noise voltage ( $S_n(f)$ ) specification by looking at the following table, where N is the last digit of the student badge number

E.g. Mr. James Bond (badge number 007) will select  $\sqrt{S_n(f)} = \sqrt{v_{iN}^2/\Delta f} < 36 \text{ nV}/\sqrt{\text{Hz}}$ .

- **Noise**

N	0	1	2	3	4
$\sqrt{S_n(f)} \text{ [nV}/\sqrt{\text{Hz}}]$	22	24	26	28	30
N	5	6	7	8	9
$\sqrt{S_n(f)} \text{ [nV}/\sqrt{\text{Hz}}]$	32	34	36	38	40

- in addition, try to minimize power consumption.

# Additional instructions and report template

- The report should be prepared with the following template:
  1. Page 1: Name, badge number, related specs, circuit schematic and table with the transistors' sizing defined in the design process by the student.
  2. Pages 2 and 3: description of the design procedure.
  3. Page 4 and following: SPICE plots (Bode plots, transient analysis, etc. . . ).
  4. Last page: table which compares the requested specs with the achieved circuit performance.
- Drop an email to: "l.demarchi@unibo.it" attaching the report (pdf), and all the SPICE files (schematics, netlists, libraries) which have been used in the simulations.
- The project task should be done autonomously.
- The project report should be delivered to the instructor one week before the scheduled oral examination.